


D-band SiGe Subharmonic Downconverter with Dynamic Conversion Gain and Fixed Input Compression

Jonathan Tao, James Buckwalter
University of California, Santa Barbara


UC Santa Barbara
Santa Barbara, California 93106

UC SANTA BARBARA


Motivation

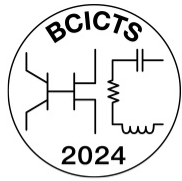

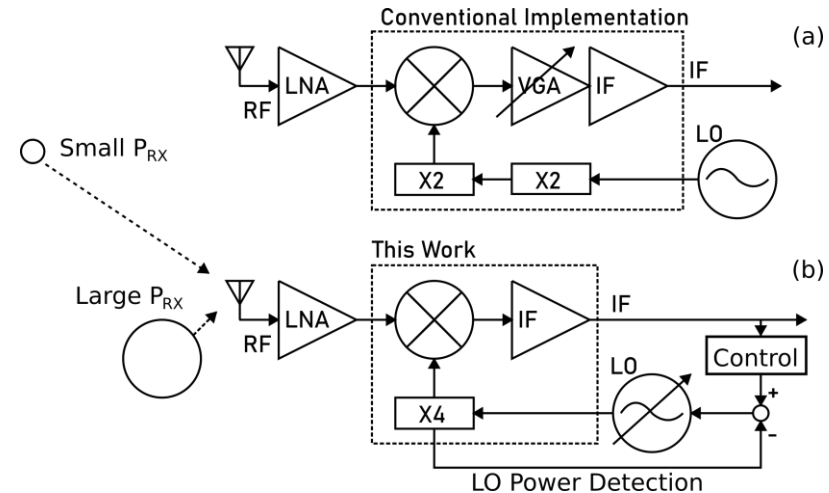- Power consumption above 100 GHz is prohibitive:
 - mobile applications
 - Radar-radio fusion on platform
- LO system power dominates receiver power consumption
- **Reduce power in LO chain dynamically with channel conditions**




Goals of This Work

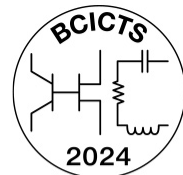



X4 Subharmonic downconverter at D-band (110 GHz – 170 GHz)

1. Linearize gain on LO frequency multiplier
 - backoff controllability to save power
2. Simplify circuit to save power and to integrate into an array

Problem: Gain Sensitivity

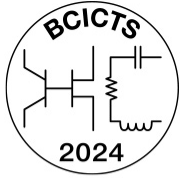


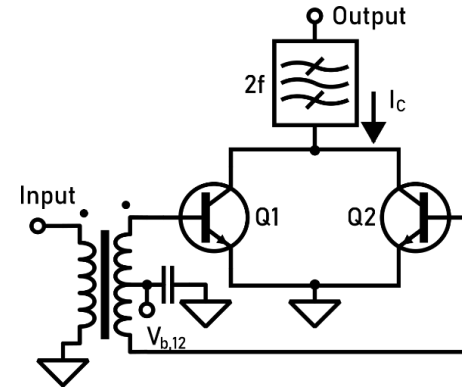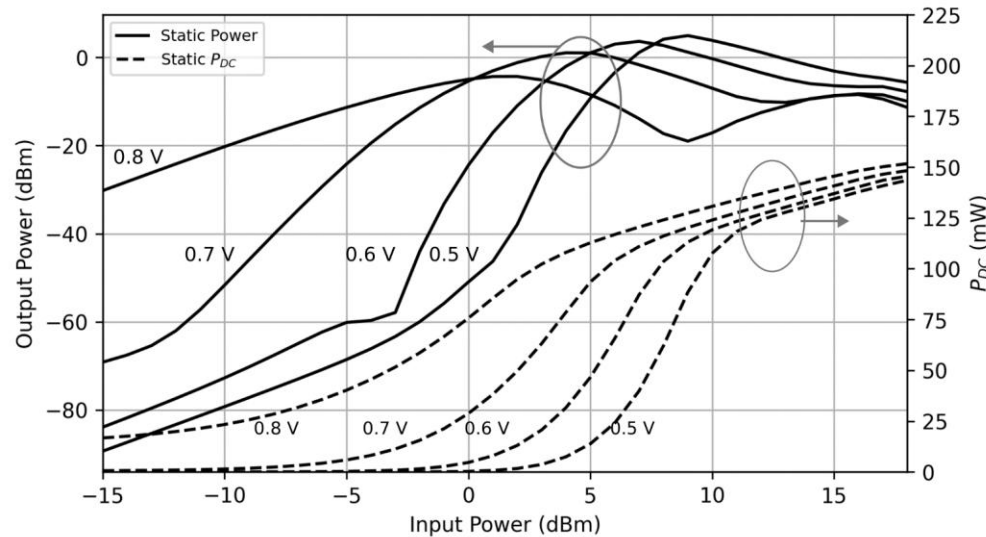- Typical multiplier chains operate at a single saturating power
- High gain sensitivity in back-off power conditions: poor controllability




Simulation on frequency doubler with different biases for optimization

Push-pull Frequency Multipliers

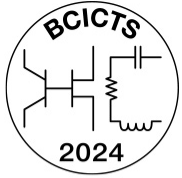



- Input is rectified to produce pulsed waveform
- We can get a 4th harmonic
- **But there is an additional DC current**
 - Affects biasing and gain
 - Causes extreme gain sensitivity to power
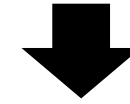
$$I_c(t) = I_0 + I_1 \cos(\omega t) + I_2 \cos(2\omega t) + \dots I_n \cos(n\omega t)$$




Fourier Series

$$I_n = I_{max} \frac{4t_0}{\pi T} \begin{cases} 1 & , \text{ if } n = 0 \\ 2 \cdot \left| \frac{\cos\left(\frac{n\pi t_0}{T}\right)}{1 - \left(\frac{n\pi t_0}{T}\right)^2} \right| & , \text{ if } n \text{ even} \\ 0 & , \text{ if } n \text{ odd} \end{cases}$$

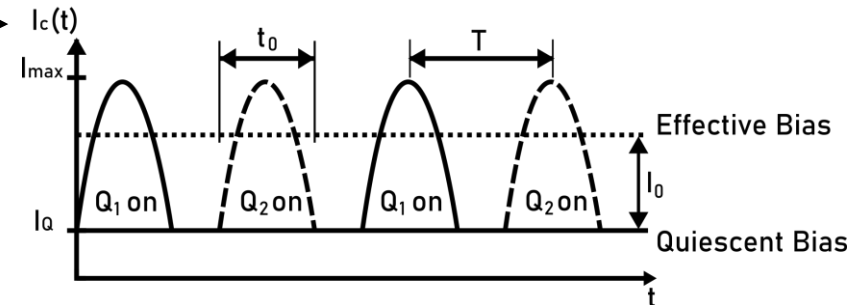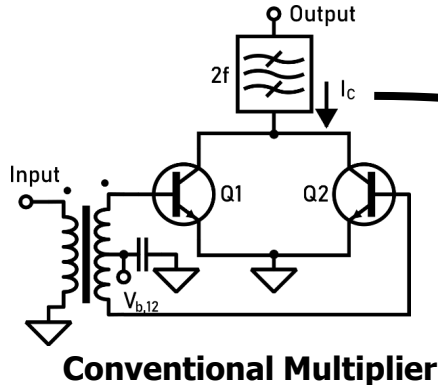


Proposed Downconverter

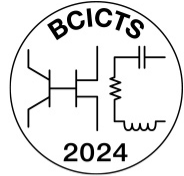

Active Load

Mixer

X4 Frequency Multiplier

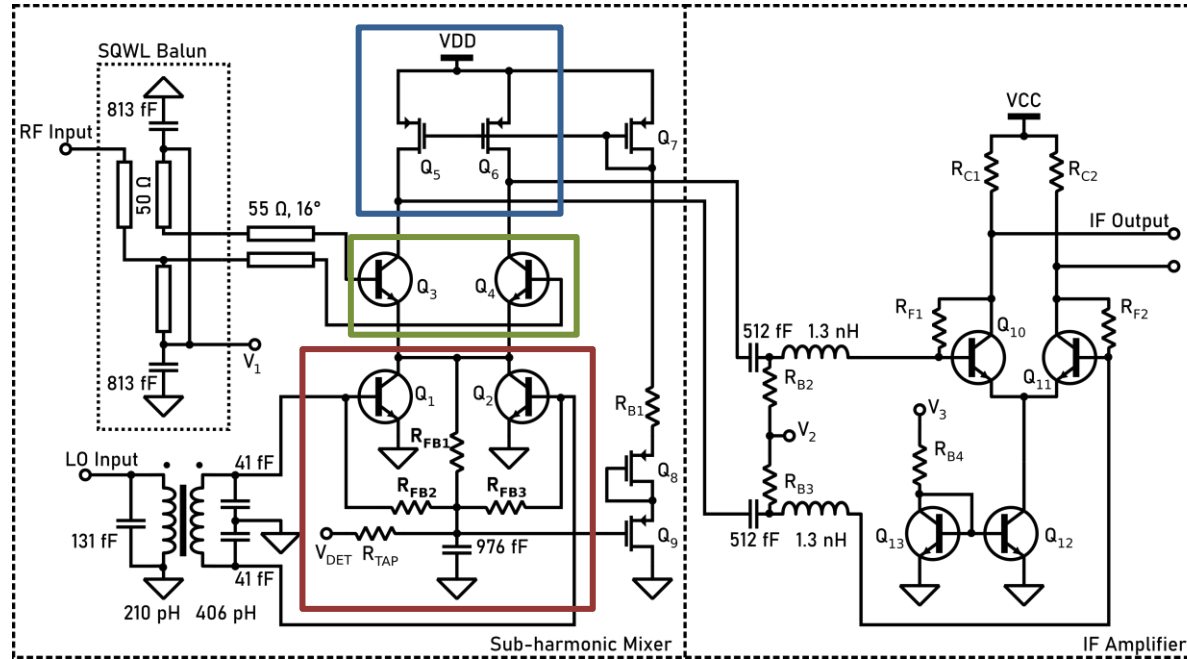


VDD	VCC	3 V
V ₁		1.5 V
V ₁	V ₃	1 V



Q ₁	Q ₂	6 μm
Q ₃	Q ₄	10 μm
Q ₅	Q ₆	0.1 × 40 μm
Q ₇		0.1 × 2 μm
Q ₈	Q ₉	0.1 × 10 μm
Q ₁₀	Q ₁₁	4 μm
Q ₁₂		6 μm
Q ₁₃		0.5 μm

R_{FB1}	1 k Ω
$R_{FB2} R_{FB3}$	3.5 k Ω
$R_{C1} R_{C2}$	200 Ω
$R_{F1} R_{F2}$	800 Ω
R_{B1}	1 k Ω
$R_{B2} R_{B3}$	5 k Ω
R_{B4}	300 k Ω
R_{TAP}	500 Ω

Feedback Bias Analysis

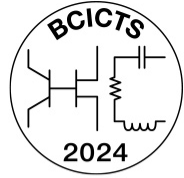

Equivalent DC Model

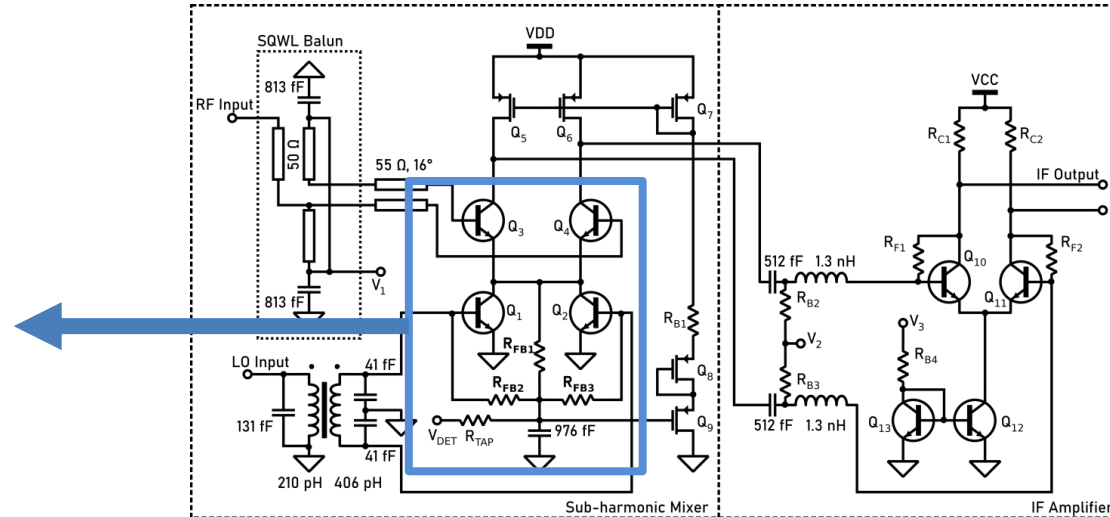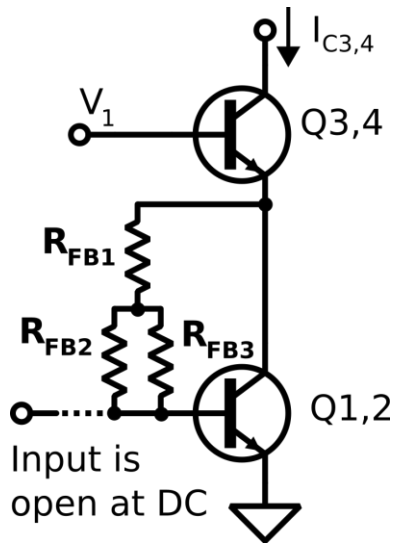


VDD VCC	3 V
V ₁	1.5 V
V ₁ V ₃ V ₂	1 V

Q ₁ Q ₂	6 um
Q ₃ Q ₄	10 um
Q ₅ Q ₆	0.1 x 40 um
Q ₇	0.1 x 2 um
Q ₈ Q ₉	0.1 x 10 um
Q ₁₀ Q ₁₁	4 um
Q ₁₂	6 um
Q ₁₃	0.5 um

R _{FB1}	1 kΩ
R _{FB2} R _{FB3}	3.5 kΩ
R _{C1} R _{C2}	200 Ω
R _{F1} R _{F2}	800 Ω
R _{B1}	1 kΩ
R _{B2} R _{B3}	5 kΩ
R _{B4}	300 kΩ
R _{TAP}	500 Ω

Proposed Design: Feedback Bias

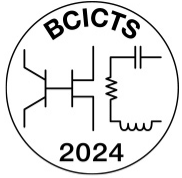

- Parallel transistors shorted at DC: treat as one
- Simplifying assumptions:


$$V_{BE1,2} \approx V_{BE3,4} \quad I_{C3,4} \approx I_{C1,2}$$

- **Feedback Bias has stable bias point:**


$$I_{C3,4} = \beta_{1,2} \frac{V_1 - 2V_{BE}}{R_{FB1} + R_{FB2} || R_{FB3}}$$

- **Current change suppressed by negative feedback on V_{BE}**


Equivalent DC Model

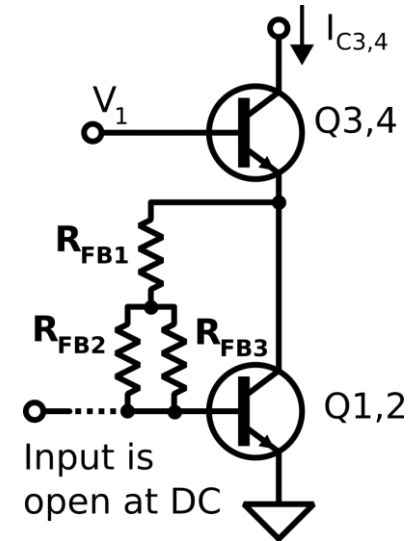


Simulated Effect of Static Biasing

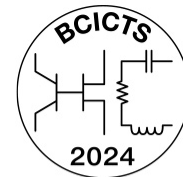

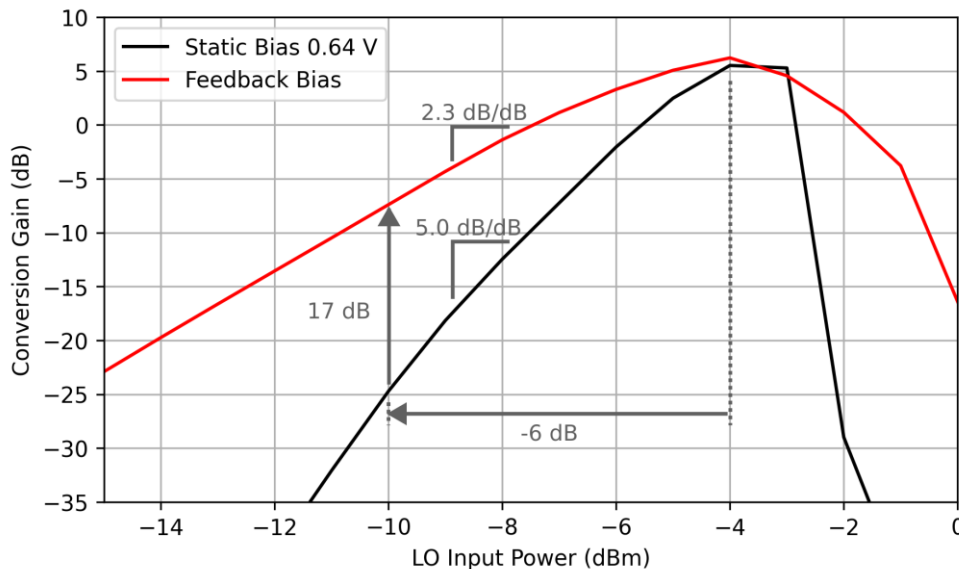
- With -6 dB LO backoff from peak gain
 - 17 dB more gain than static biased version
- Obtain higher performance at back-off and less sensitive gain




Layout

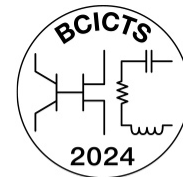

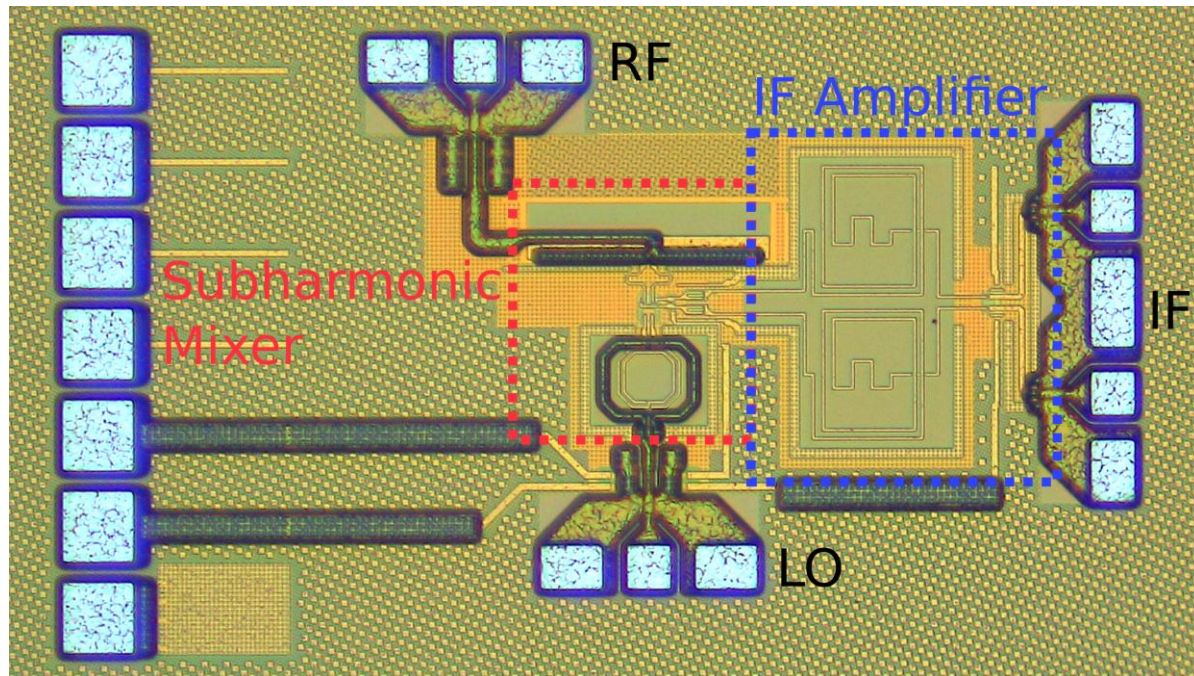
- Global Foundries 9HP+
 - 90-nm SiGe BiCMOS
- Core: 0.56 mm x 0.35 mm




Measurement

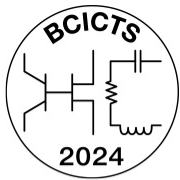



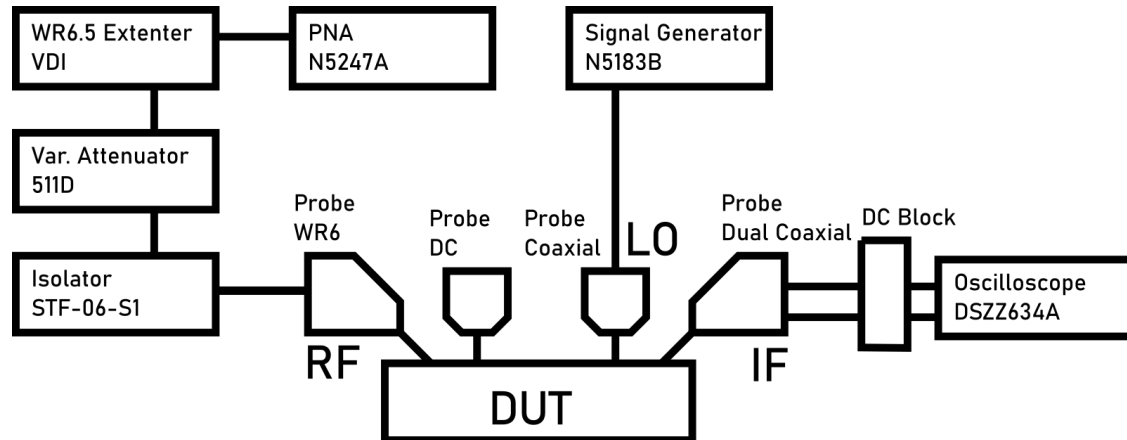
- Results calibrated with reference power meter (scalar measurement)
- Differential mismatch compensated with time delay in oscilloscope




Conversion Gain Over Frequency

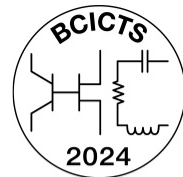

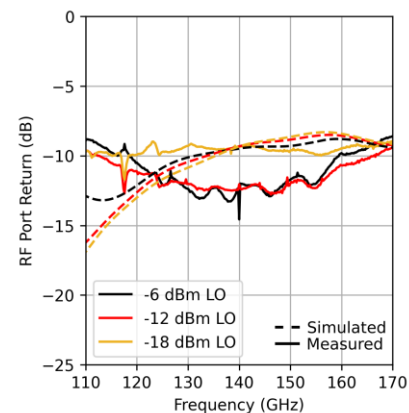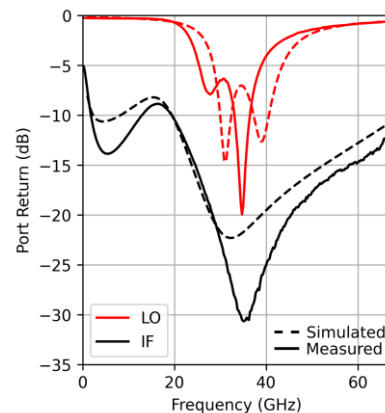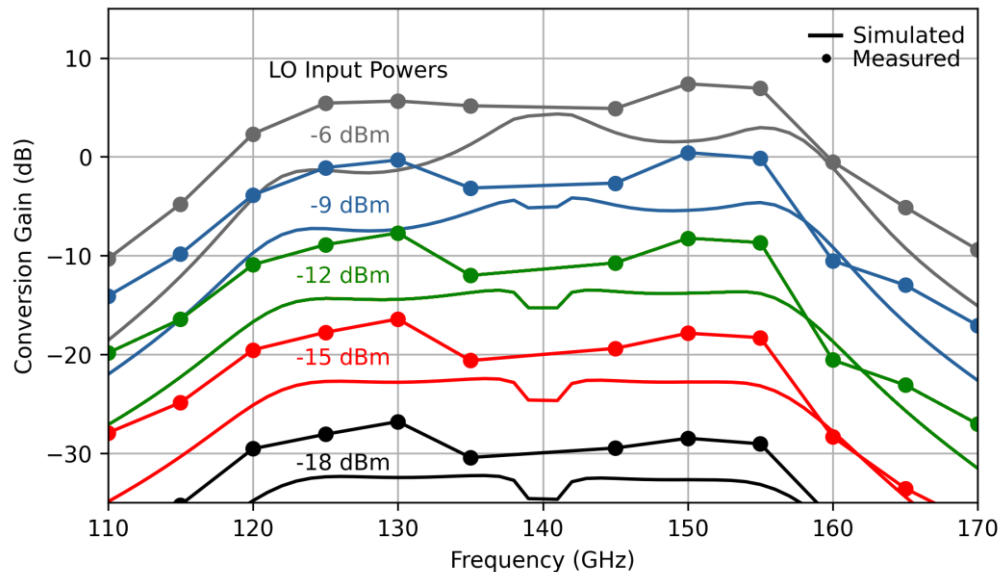
- Reliable control of conversion gain over a wide LO power range
- LO port frequency shift led to better match at target LO frequency



Power Consumption Tradeoff

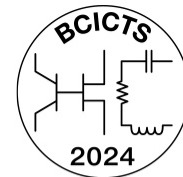


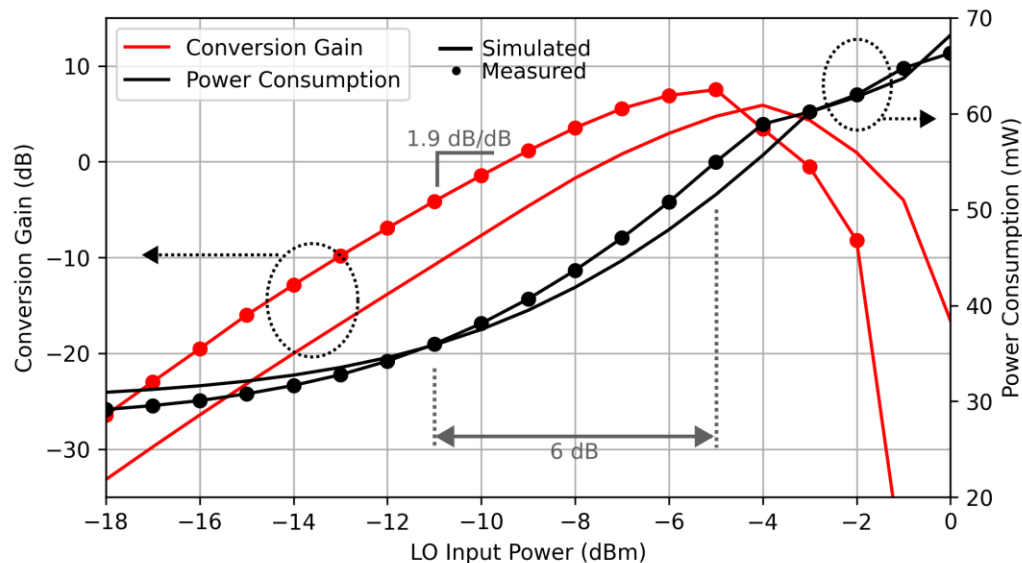- Back off LO power from -5 dBm to -11 dBm
 - **Trade 11.7 dB of gain to save 35% power**




155 GHz RF with 140 GHz LO


Compression and Power Detector

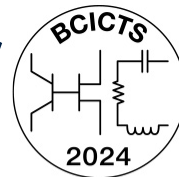

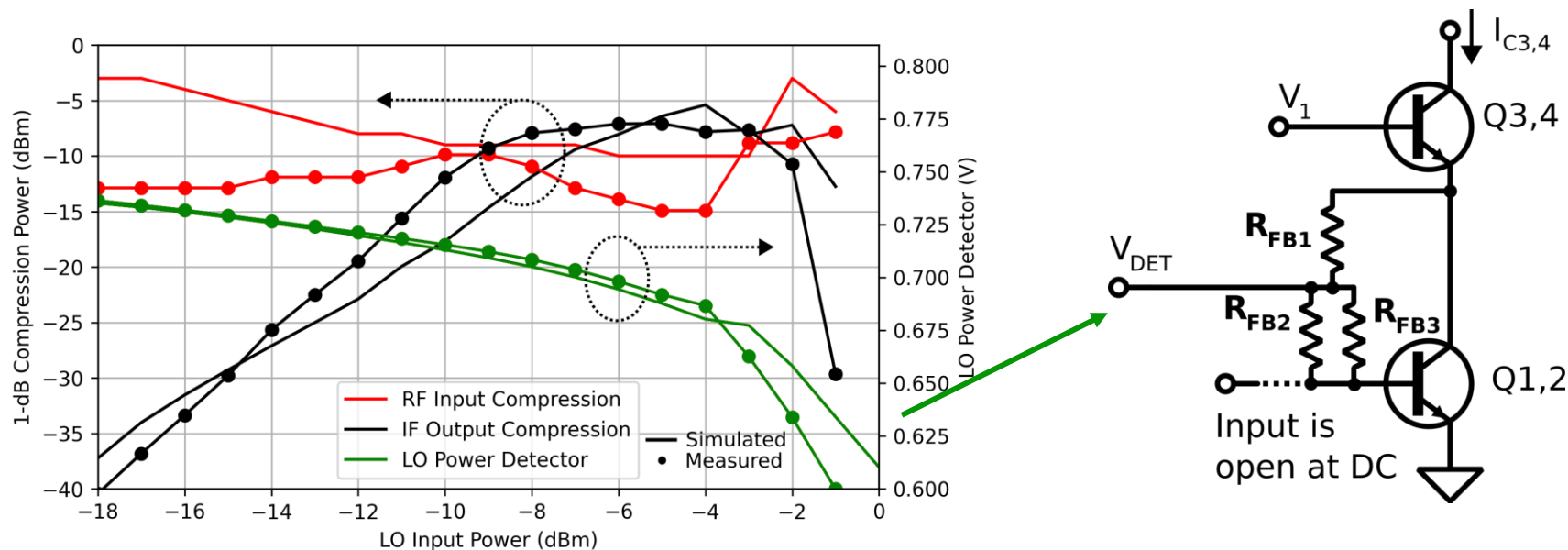- Input compression is insensitive to LO power variation
- Feedback bias circuit can be used for LO power detection



Conclusion

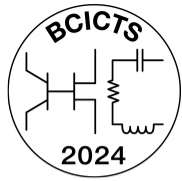


- A fourth subharmonic D-band downconverter is implemented with bias feedback
 - Demonstrates reliable LO power backoff to save power
- Achieves a high multiplication factor without sacrificing additional area, power consumption, or LO power requirement

Reference	This Work	[3]	[6]	[7]
Technology	90-nm SiGe	90-nm SiGe	130-nm SiGe	130-nm SiGe
Subharmonic	4	2	2	1
f_C (GHz)	140	136	121	140
BW_{3dB} (GHz)	35	38	>14	35
Gain (dB)	7.5	5.1	4	32
P_{1dB} (dBm)	-15	-7	-	-41
Noise Figure (dB)	21.7*	-	23*	9.5
LO (dBm)	-5	2	7	-2
P_{DC} (mW)	55	51	89	65
Area (mm ²)	0.196 [†]	0.450 [†]	-	0.191 [†]

* Simulated [†] Area without pads.

Acknowledgements

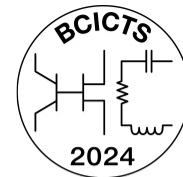

- This work was supported by the Semiconductor Research Corporation (SRC) under the JUMP program, Cognisense
- The authors appreciate the support of GlobalFoundries for access to the 9HP+ process.




**Semiconductor
Research
Corporation**



GlobalFoundries™

Comparison References

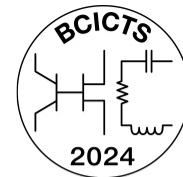

[3] A. Moradinia, Y. A. Mensah, B. L. Ringel, and J. D. Cressler, "A 117–155-GHz SiGe HBT D-Band Subharmonic Mixer Utilizing a Novel 180° Hybrid Coupler," IEEE Microwave and Wireless Technology Letters, vol. 33, no. 6, pp. 731–734

[6] K. Schmalz, W. Winkler, J. Borngraber, W. Debski, B. Heinemann, and J. C. Scheytt, "A Subharmonic Receiver in SiGe Technology for 122 GHz Sensor Applications," IEEE Journal of Solid-State Circuits, vol. 45, no. 9, pp. 1644–1656,

[7] T. Maiwald, J. Potschka, K. Kolb, M. Dietz, A. Hagelauer, A. Visweswaran, and R. Weigel, "A Broadband Zero-IF Down-Conversion Mixer in 130 nm SiGe BiCMOS for Beyond 5G Communication Systems in D-Band," IEEE Transactions on Circuits and Systems II: Express Briefs, vol. 68, no. 7, pp. 2277–2281